



Microwave Characterization Center

Chalmers Winter School - GaN Power amplifiers

January 16th, 2020


SUMMARY :

- I. Quick MC2-Technologies Introduction
- II. OMMIC GaN processes
- III. 20W Ku-Band HPA Example
- IV. 0.5W W-Band PA Example





- Microwave Characterization Center (MC2)
- Spinoff from IEMN laboratory, Lille-métropole
- Created in 2004 by:
 - Nicolas Vellas, Ph.D (CEO)
 - Christophe Gaquière, Pr. (CTO)
- > 50 employees
- Involved in several European R&D projects :
 - H2020 Spiders
 - H2020 ALADIN
 - H2020 GRACE
- Turnover 2019: 8M€

 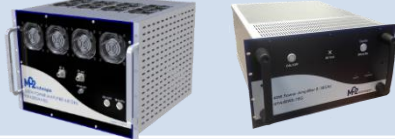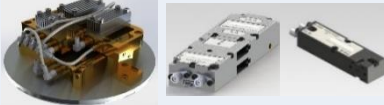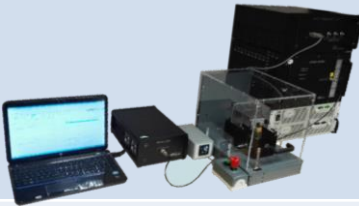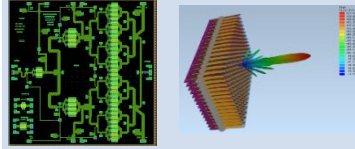

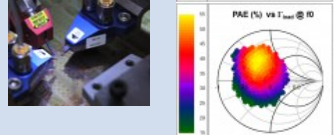



- New facilities in 2020 !



Security Products	
MM-Imager	
UAV Scrambler	
Microwave shield meter	

Microwave Products	
Amplifiers	
TR modules mmW	
Pulsed IV system 1000V/20A	
Efuse, Bias tee, Kit SMM	

Services	
Design MMIC Hybrid & antenna	
Prototyping	
Characterization	
Reliability tests	

- GaAs and GaN MMIC (PA, LNA, Mixers...)
- OMMIC, UMS, WIN processes

Permanent R&D Program on products and services (H2020, ANR)

OMMIC Processes

Process	ED02AH	D01PH	D01MH	D007IH	D01GH	D006GH
Technology	GaAs p-Hemt	GaAs p-Hemt	GaAs m-Hemt	GaAs m-Hemt	GaN on Si/SiC	GaN on Si/SiC
Status	Production	Production	Production	Production	Preproduction	Development
Space Grade	Space Qualified	Space Qualified	Space Qualified	In 2020	In 2020	-
Gate Length (μm)	0.18	0.135	0.125	0.07	0.1	0.06
Wafer Size (")	3	3	3	3	3	3
Thickness (μm)	100	70 100	70 100	70 100	100	100
Gate Write	E-beam	E-beam	E-beam	E-beam	E-beam	E-beam
Ft (GHz)	60	100	150	300	110	170
Fmax (GHz)	110	180	250	450	160	250
Vbgd (V)	8	12	8	4	40	25
Vds max (V)	7	10	6	3	25	20
Idss (mA/mm)	250(on)/140(off)	500	300	200	700	800
Idss max (mA/mm)	400(on)/180(off)	700	500	400	1100	1200
MIM Capacitors (pF/mm ²)	49 & 400	400	400	400	400	400
NF (dB)	0.8 (18 GHz)	1.1 (GHz)	0.8 (30 GHz)	0.5 (30 GHz)	1.5 (40 GHz)	1 (50 GHz)
Power Density (mW/mm)	330	640	300	NA	3300	2000
gm (mS/mm)	450	650	700	1600	650	700

OMMIC GaN on Si
Process D01GH


- D01GH
 - 100nm gate length
 - Ft/Fmax = 110/160GHz
 - 3300mW/mm power density
- D006GH
 - 60nm gate length
 - Ft/Fmax = 170/250GHz
 - 2000mW/mm power density

- Higher VDS and IDSS -> Higher power density than GaAs for similar frequency of operation
- Also more power to dissipate

20W Ku-Band HPA Example

Process D01GH


 
- Bias point and transistor performances
- PA topology
- Zoom on output combining
- Stability
- Measurement results



Targeted Ku-Band PA performances

- Freq= 15-18GHz
- $P_{sat} \geq 43\text{dBm}$ (20W) for $4 \times 2.8\text{mm}^2$ PA
- PAE $\geq 30\%$
- Power Gain $\geq 20\text{dB}$

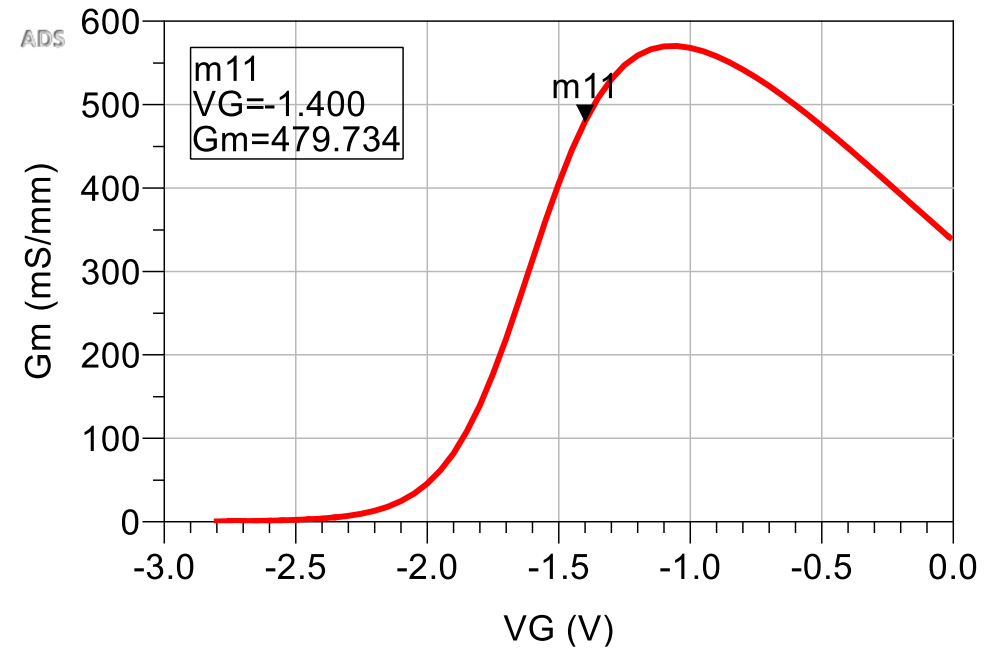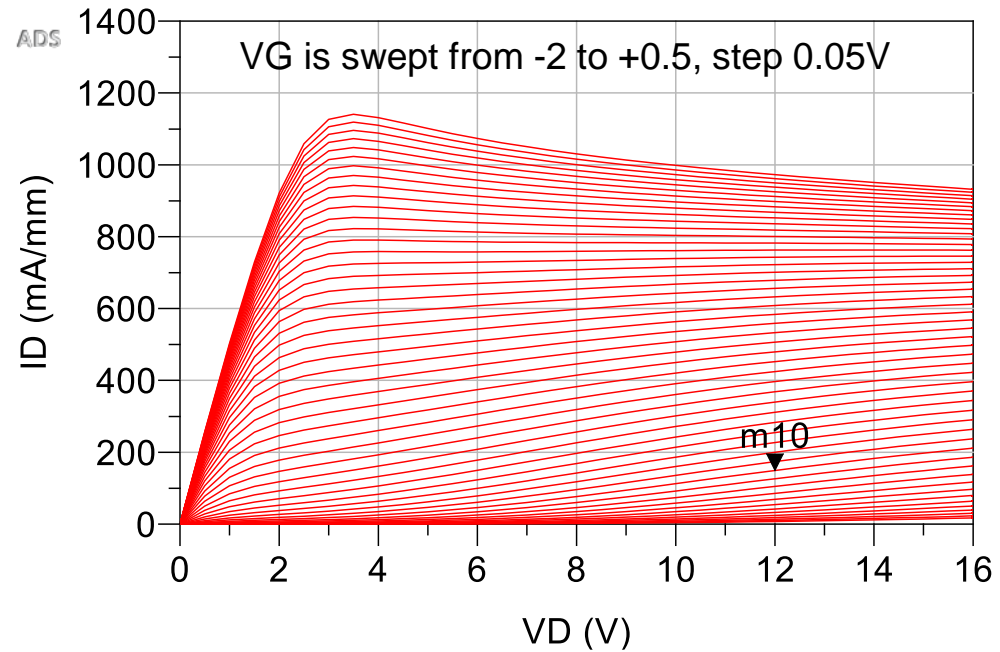
m10
VD=12.000
ID_mA_per_mm=149.223
VG=-1.400



- Drain bias voltage is $VD = 12V$ (recommended)
- Gate bias voltage is $VG = -1.4V$,
- AB class, usual trade-off between gain and efficiency

Ku-Band PA – Transistor performances

 Load-Pull simulation @4dB compression, 8x150um



indep(PAE_contours_p) (0.000 to 36.000)
 indep(Pdel_contours_p) (0.000 to 32.000)

- F=16GHz
- Pout step=0.5dB
- PAE step=4%


Maximum Power-Added Efficiency, %

54.75



Maximum Power Delivered, dBm


37.45

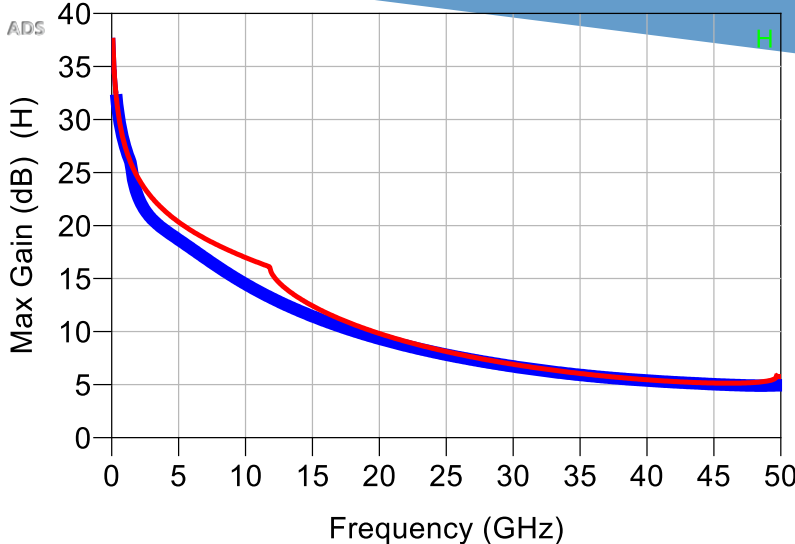36.5dBm (single transistor Pout after trade-off) +9dB (combining per 8) - 1dB (combining losses) -> **Pout > 44dBm is expected**



 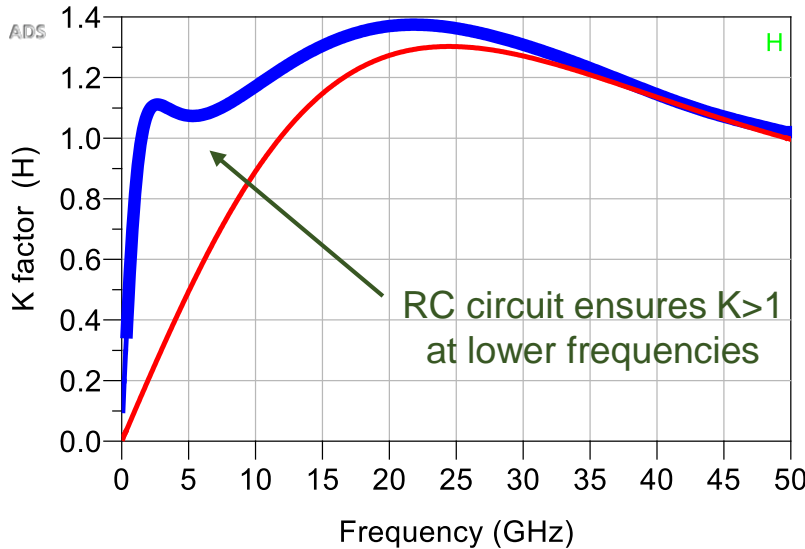
- 8x150um transistor alone
- 8x150um transistor with gate RC circuit
- Max gain is 10dB



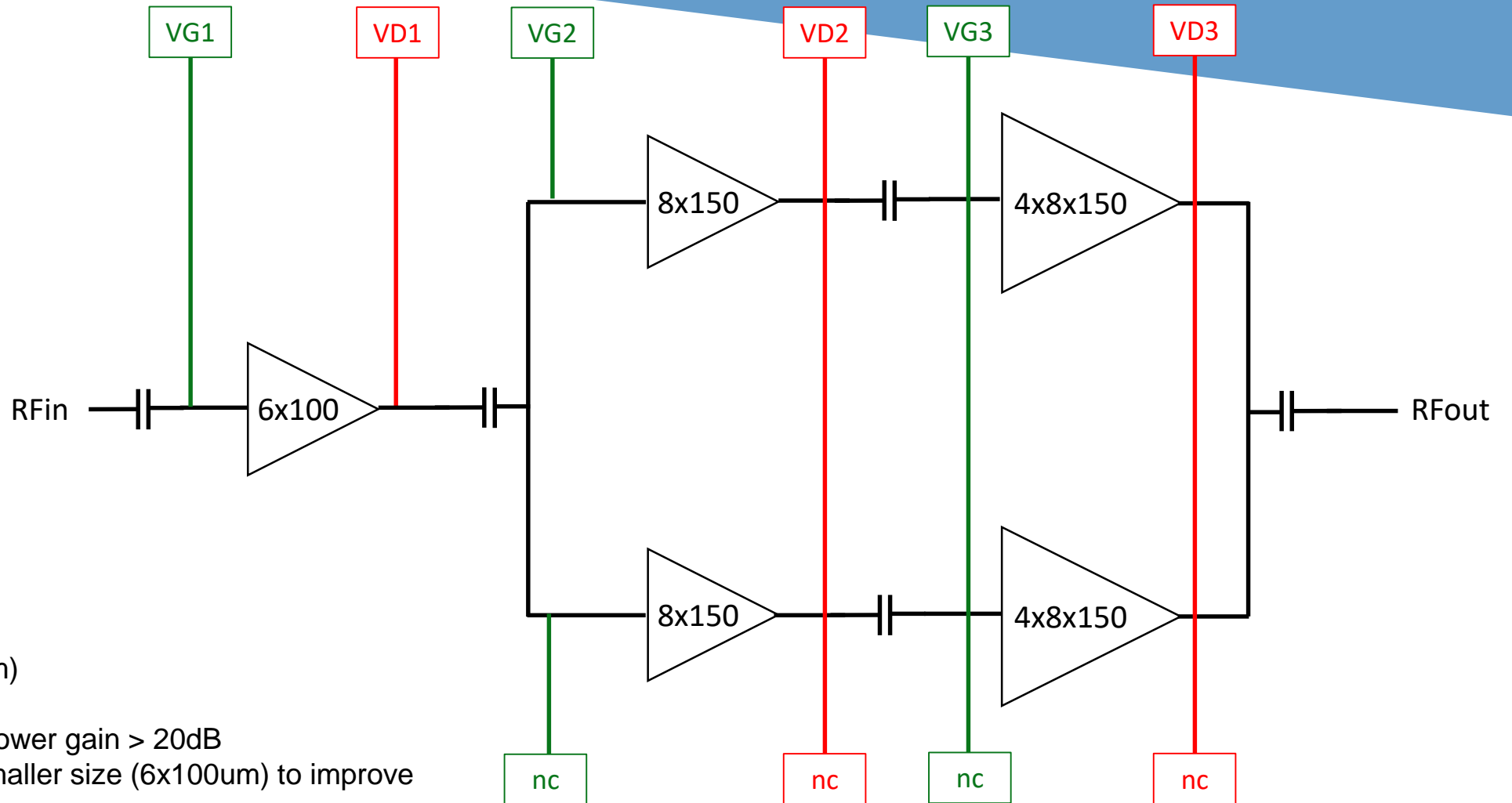


- $VD=12\text{ V}$
- $VG=-1.4\text{V}$ (150mA/mm)
- 3 stages needed for power gain $> 20\text{dB}$
- Input transistor has smaller size (6x100um) to improve gain

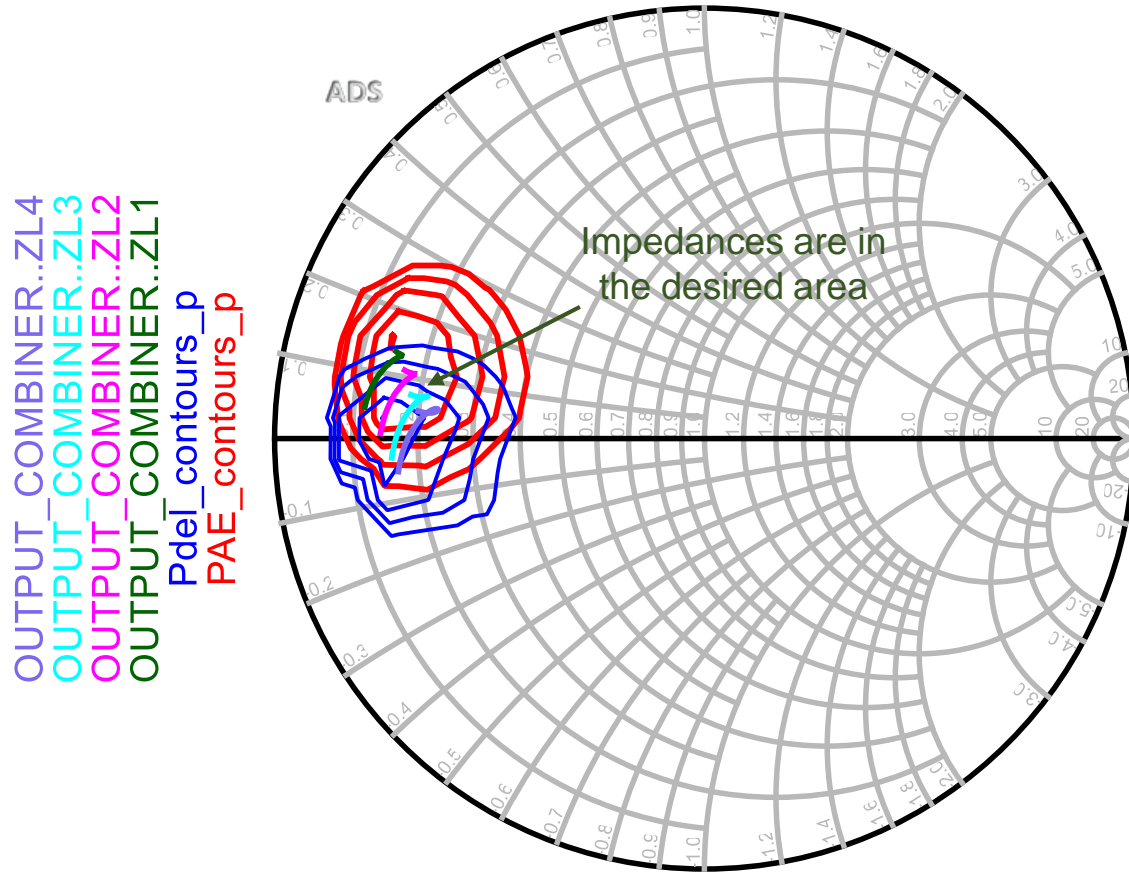Load-Pull simulation @4dB compression, 8x150um and actual load impedances of output transistors




OUTPUT_COMBINER..ZL4
 OUTPUT_COMBINER..ZL3
 OUTPUT_COMBINER..ZL2
 OUTPUT_COMBINER..ZL1
 Pdel_contours_p
 PAE_contours_p

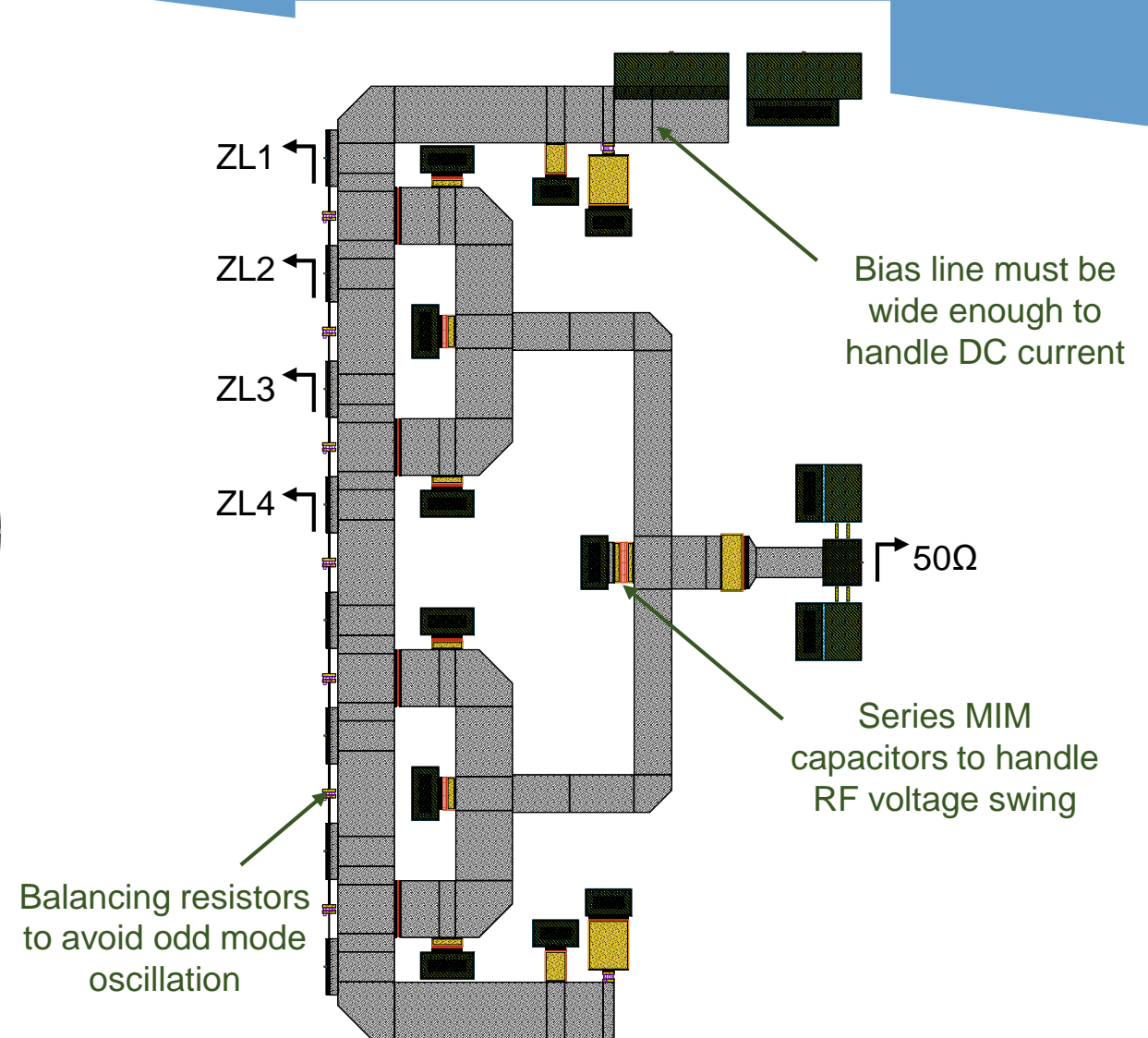indep(PAE_contours_p) (0.000 to 36.000)
 indep(Pdel_contours_p) (0.000 to 32.000)
 freq (14.00GHz to 18.00GHz)




Example K analysis for PA stage 2, VG sweep

Stage 2 Stability

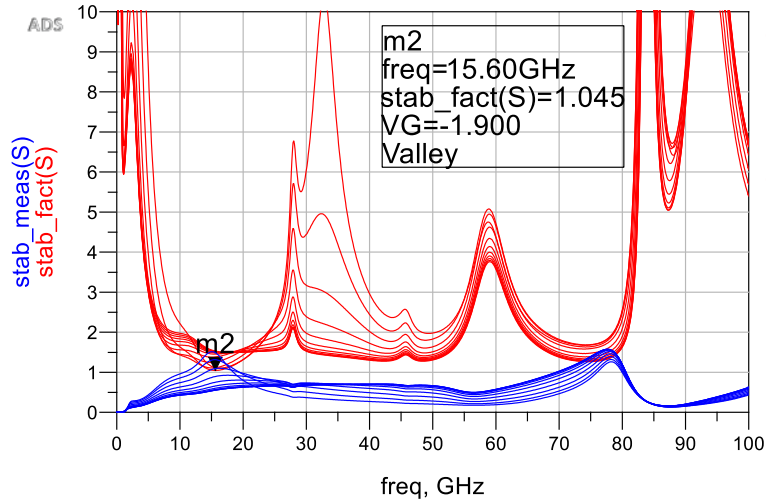


 - Small signal analysis
- K should be >1 for unconditional stability



Example Poles/Zeros analysis for PA





Poles/Zeros

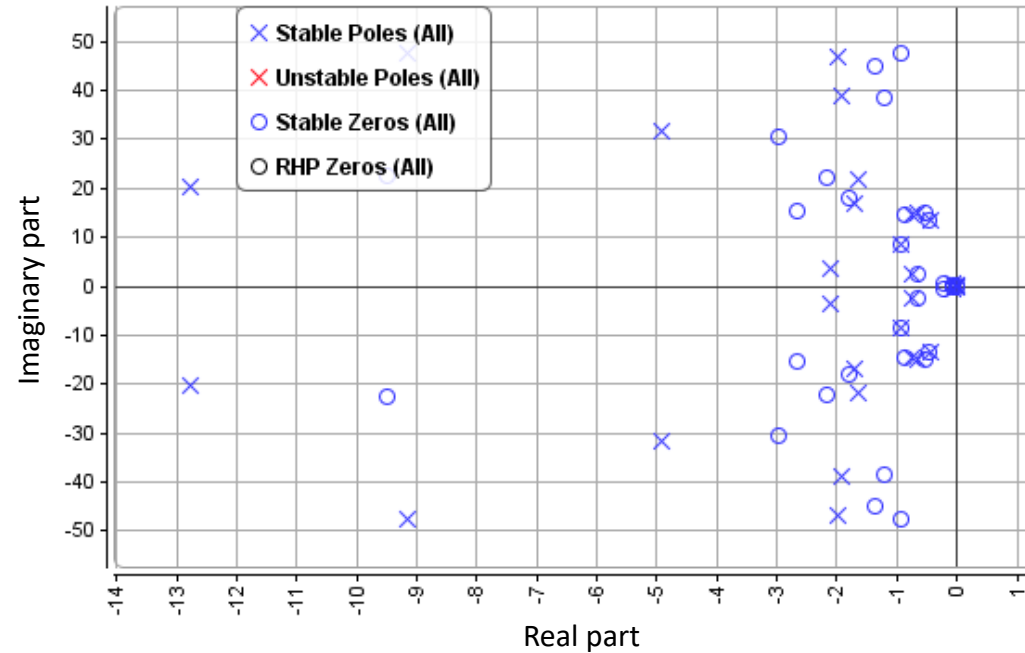

- Poles with positive real part mean instability
- Oscillation frequency is given by imaginary part
- Input power can be swept (large signal analysis)

- Stability analysis is mandatory for amplifiers, up to Ft
- Different analysis are recommended: Rollet factor (K factor) for each stage, Transient, Pole/Zero analysis...

Ku-Band PA – S-Parameters Measurements

 
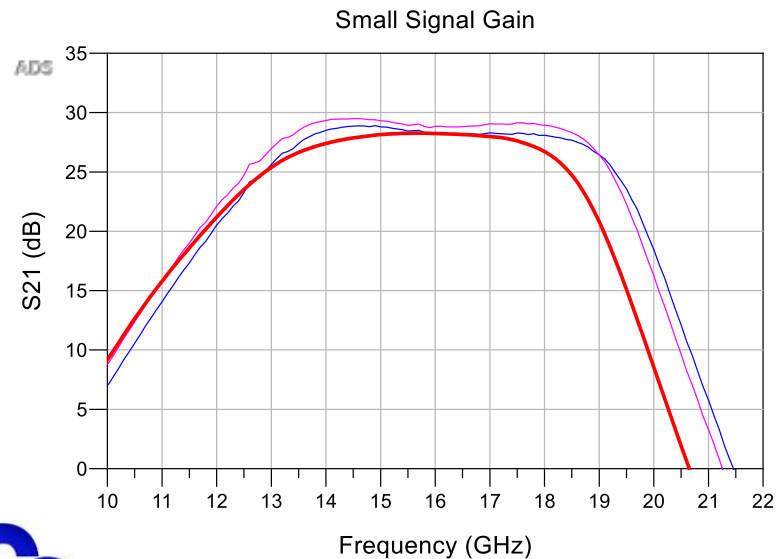
 
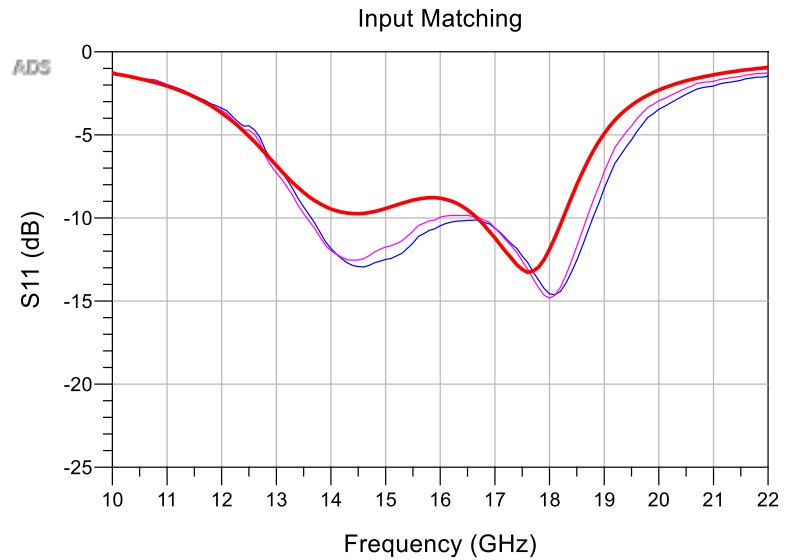


- $V_D=12\text{ V}$
- $I_{D0}=1950\text{ mA}$
- CW stage 1
- Pulsed stages 2&3 (5%, 100us)

- Simulation
- MMIC 1
- MMIC 2

- Matching is better than -10dB in 14-18GHz band
- Small signal gain is 28dB
- Slight shift versus simulation

Ku-Band PA – Power Measurements

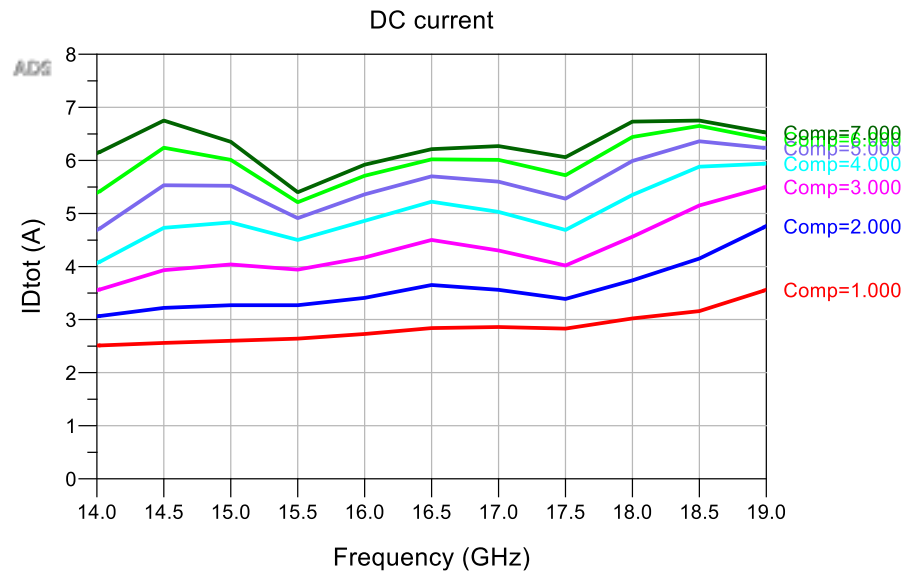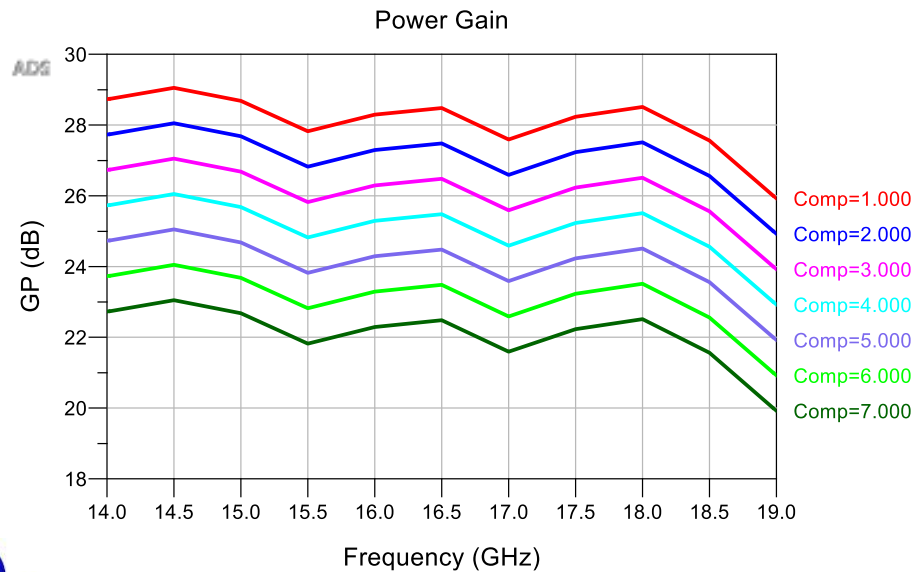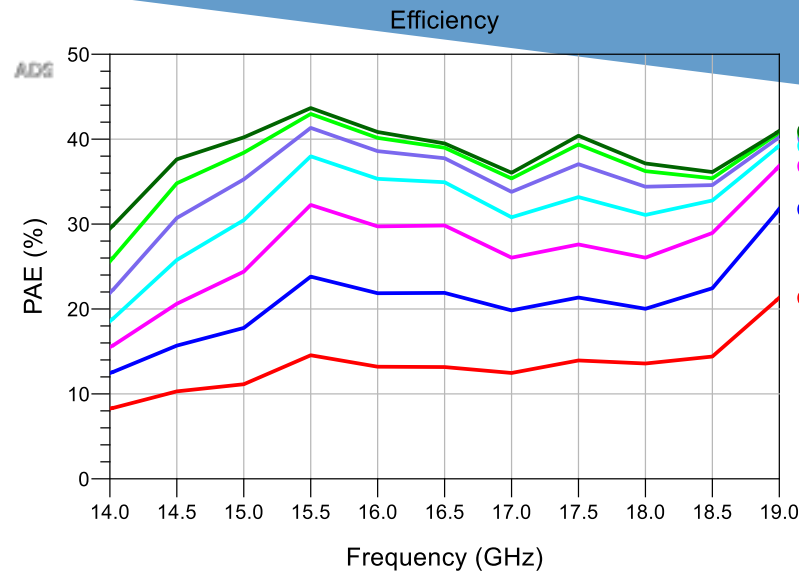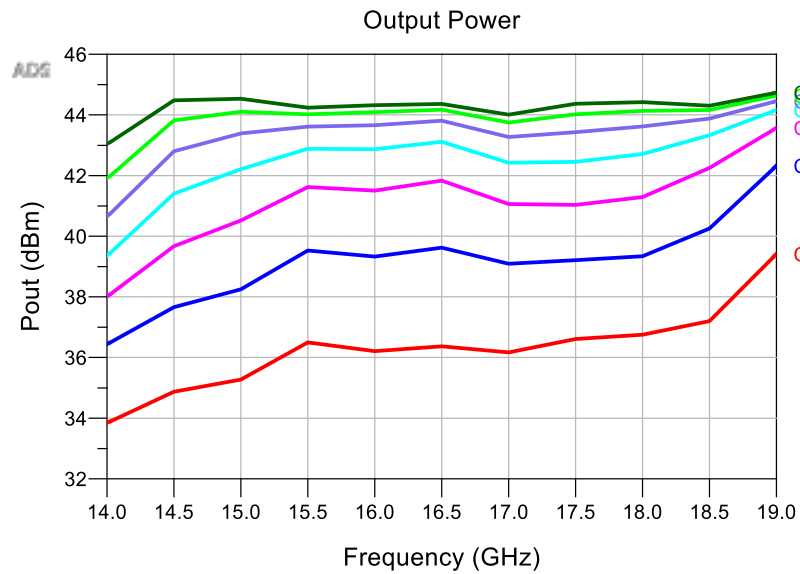


- VD=12 V
- VG=-1.4 V
- CW stage 1
- Pulsed stages 2&3 (0.5%, 20us)
- Measured output power is 44dBm with PAE > 35% and GP > 20dB
- High level of compression needed to reach Psat

0.5W W-Band PA Example

-

Process D006GH


 
- Bias point and transistor choice
- PA topology
- Lange couplers
- Measurement results



Targeted W-Band PA performances


- Freq= 93-100GHz
- Psat \geq 27dBm (0.5W)
- Power Gain \geq 10dB

  m10
VD=12.000
ID_mA_per_mm=288.279
VG=-1.250



- Drain bias voltage is 12V
- Gate bias voltage is near maximum gm for highest gain
- ID is below 300 mA/mm to keep dissipated power below maximum recommended value (3.5 W/mm)

 
Load-Pull simulation @2dB compression, 2x30um




indep(PAE_contours_p) (0.000 to 34.000)
indep(Pdel_contours_p) (0.000 to 84.000)
freq (500.0MHz to 150.0GHz)


- F=97GHz
 - Pout step=1dB
 - PAE step=2%
 - Gain step=0.5dB
- | | Maximum Power-Added Efficiency, % | Maximum Power Delivered, dBm |
|--|-----------------------------------|------------------------------|
| | 37.10 | 23.58 |

 - Optimum impedance area is close to the edge of the Smith chart and very selective -> Maximum delivered power per transistor will be around 20dBm -> 8 transistors are needed to reach Pout > 27dBm




 - 2x30um transistor alone
- Max gain is 6.5dB at 100GHz
- Stability is unconditional from 60 to 130GHz






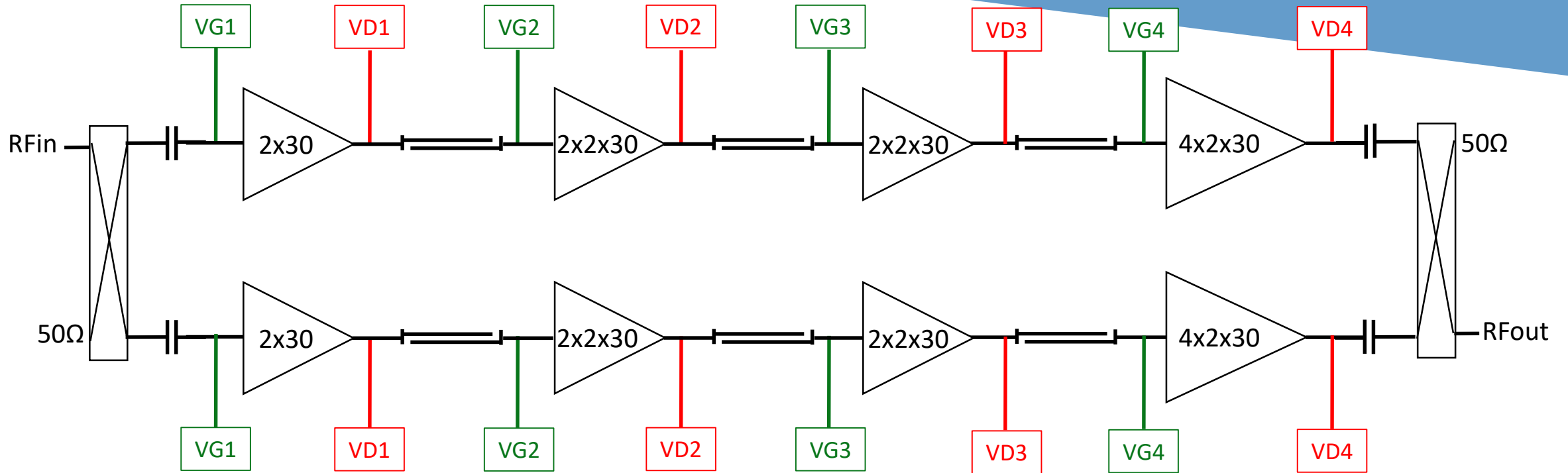

 - VD=12 V
- VG=-1.25V (300mA/mm)
- 4 stages needed for usable power gain
- Lange couplers used for good input/output matching and isolation between north and south amplifier branches



 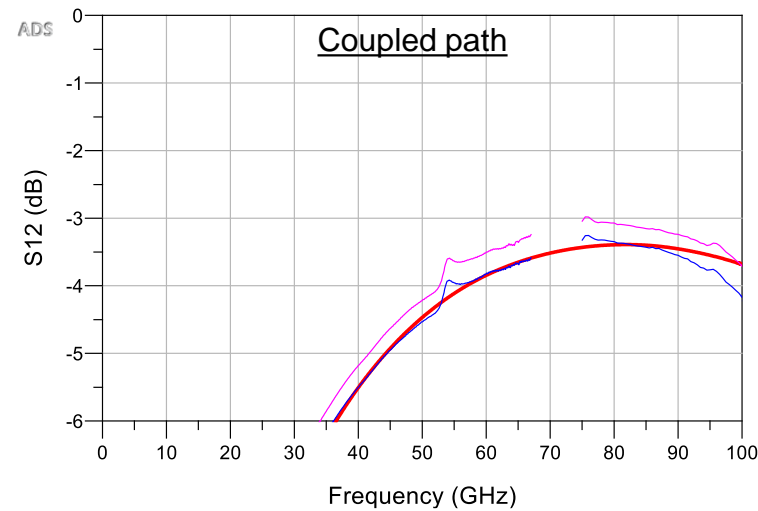 
- TRL calibration
- EM Simulation
- Measurement (Ret 1805)
- Measurement (Ret 1813)




- TRL calibration to remove GSG pad impact on measurement
- Measured (TRL) Back to Back Lange couplers losses are around 1dB
- In line with simulation

W-Band PA – S-Parameters Measurements


Input Matching

 


Reverse Isolation

 

Small Signal Gain

 

Output Matching

 


- VD=12V,
- Nominal bias: 300mA/mm, 3.6W/mm
- Total dissipated power in pulse is 3.9W
- Stage 0&1 are CW
- Stage 2&3 are pulsed (50us, 5%)

- Simulation
- MMIC 1
- MMIC 2
- MMIC 3
- MMIC 3


- Small signal gain is around 15dB
- Input and Output Matching are better than -10dB
- Mostly In line with simulation

W-Band PA - Power Measurements


Output Power

 

Power Added Efficiency

 

Power Gain

 

- VD=12V,
- Nominal bias: 300mA/mm, 3.6W/mm
- Stage 1&2 are CW
- Stage 3&4 are pulsed (50us, 5%)
- Dots: Measurement
- Line: Simulation

- Pout is > 27dBm in 93-97GHz band (P6dB)
- PAE is around 9%
- GP is around 10dB (P6dB)
- Measured output power level is close to expected level, though power performances are a bit narrower than simulation



Thank you !